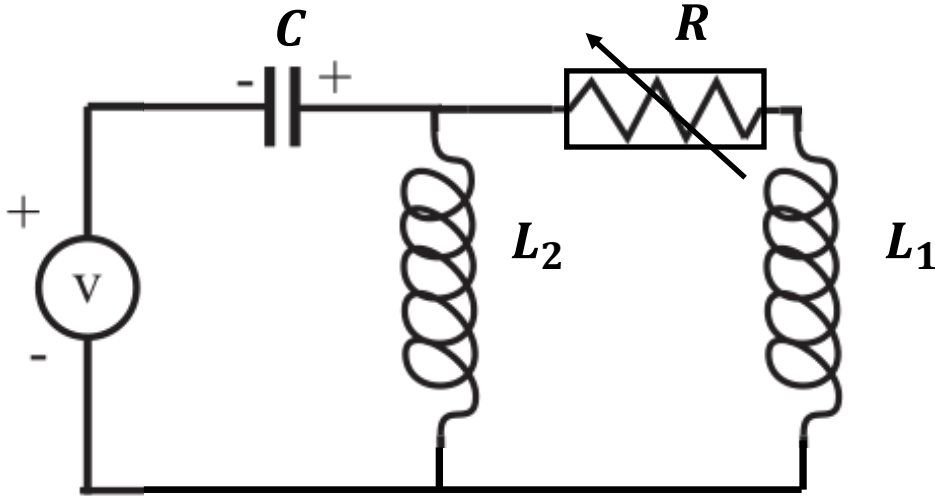


Part II: Modeling problem

Instructions:

1. Use MATLAB to solve the problem if needed;
2. Please submit the published pdf file ONLY.
3. Please use `function_name` in the end of your main script for displaying your nonlinear function. (i.e. all the functions that are written in separate files should be displayed with `type` command)



For the circuit with the nonlinear resistor satisfying the nonlinear dependence of the resistor's voltage V_R as a function of its current I where:

$$V_R = RI - RI^3, R = 1\Omega, C = 1F, L_1 = L_2 = 1H$$

- a) Write a state space model $\dot{x} = f(x, V)$ using Kirchhoff equations. Choose the inductors currents and the capacitor's voltage as state variables (i.e. $x_1 = i_{L1}, x_2 = i_{L2}, x_3 = v_c$) and choose the current over L_1 as the output (i.e. $y = x_1$).
- b) Find ALL equilibrium points for the constant input voltage V^{eq} ;
- c) Around which equilibrium points is the linearized model unstable and which is stable? Why? Check the eigenvalues for each equilibrium state.
- d) Simulate and compare the linearized and the nonlinear system using MATLAB.
- e) Demonstrate stability and instability around each equilibrium point of both the linear and nonlinear models for the same initial conditions and the same input.
- f) Is your model valid? Use circuit analysis of both the linear and nonlinear system models to explain the steady state and transient behavior.