

# Homework 6

## ECES 511

Damien Prieur

For the Following problems, **manually** calculate the expression for the response then **validate** your answer with MATLAB Simulation. Ex. If you get the response of the system  $y(t) = e^{-t}$ , please build your system in MATLAB and compare the output obtained from the system with  $y(t) = e^{-t}$  in one plot for verification.

### Problem 1

Find the response of the output variable

$$y = 2x_1 + x_2$$

in the system described by state equations

$$\dot{x}_1 = -2x_1 + u$$

$$\dot{x}_2 = x_1 - x_2$$

for a constant input  $u(t) = 5$  for  $t > 0$ ,  $x_1(0) = 0$ , and  $x_2 = 0$ .

First we rewrite the equation to be in the form

$$\dot{\mathbf{x}}(t) = \mathbf{A}\mathbf{x}(t) + \mathbf{B}u(t)$$

$$\dot{\mathbf{y}}(t) = \mathbf{C}\mathbf{x}(t) + \mathbf{D}u(t)$$

$$\mathbf{A} = \begin{bmatrix} -2 & 0 \\ 1 & -1 \end{bmatrix} \quad \mathbf{B} = \begin{bmatrix} 1 \\ 0 \end{bmatrix} \quad \mathbf{C} = \begin{bmatrix} 2 & 1 \end{bmatrix} \quad \mathbf{D} = \begin{bmatrix} 0 & 0 \end{bmatrix}$$

$$\mathbf{x}(t) = e^{\mathbf{A}t}\mathbf{x}(0) + \int_0^t e^{\mathbf{A}(t-\tau)}\mathbf{B}u(\tau)d\tau$$

$$e^{\mathbf{A}t} = \begin{bmatrix} e^{-2t} & 0 \\ e^{-t} - e^{-2t} & e^{-t} \end{bmatrix}$$

$$e^{\mathbf{A}(t-\tau)}\mathbf{B}u(\tau) = \begin{bmatrix} 5e^{-2(t-\tau)} \\ 5e^{-(t-\tau)} - 5e^{-2(t-\tau)} \end{bmatrix}$$


Since  $x(0) = 0$  we only need to evaluate the integral.

$$x(t) = \int_0^t \begin{bmatrix} 5e^{-2(t-\tau)} \\ 5e^{-(t-\tau)} - 5e^{-2(t-\tau)} \end{bmatrix} d\tau = \frac{5}{2} \begin{bmatrix} 1 - e^{-2t} \\ e^{-2t}(e^t - 1)^2 \end{bmatrix}$$


Since  $\mathbf{D}$  is zero we can find  $\mathbf{y}$  with  $\mathbf{y} = \mathbf{C}\mathbf{x}(t)$

$$\mathbf{y}(t) = \mathbf{C}\mathbf{x}(t) = \frac{5}{2}(3 - e^{-2t} - 2e^{-t})$$
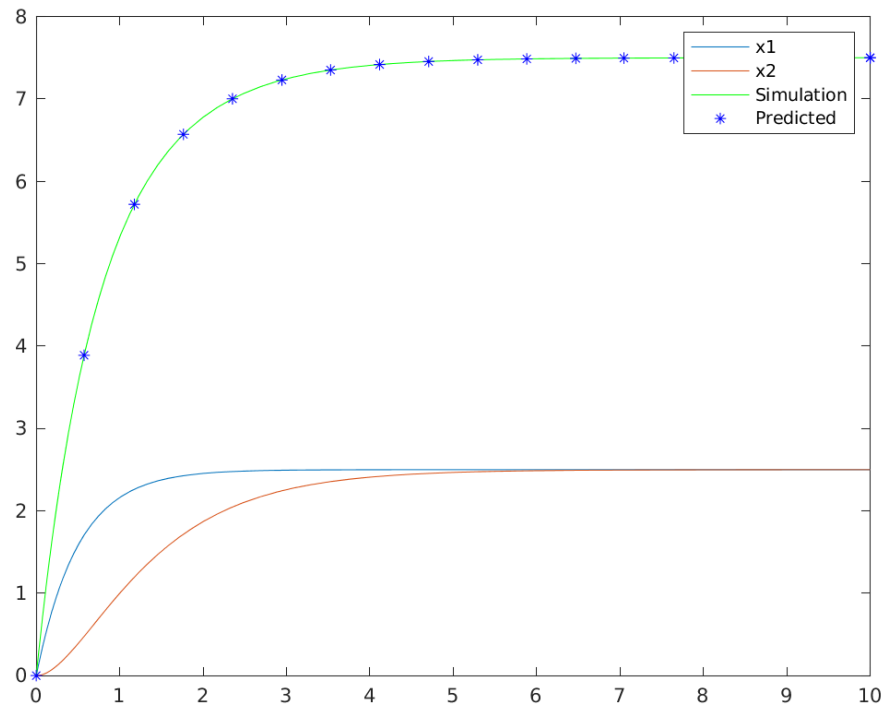
$$\mathbf{y}(t) = \frac{5}{2}(3 - e^{-2t} - 2e^{-t})$$



## Problem 2

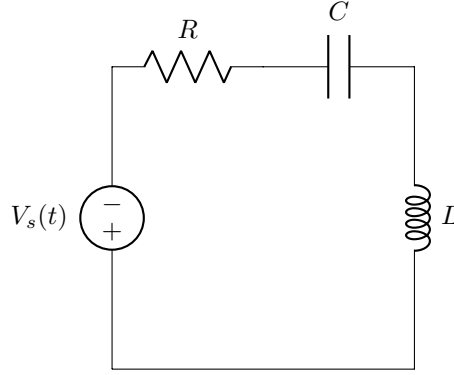

Given the standard RLC circuit ( $R = 1.2$ ,  $C = 1$ ,  $L = 0.2$ ). To build the state space equations, we choose capacitor voltage  $v_c(t) = x_1(t)$  and inductor current  $i_l(t) = x_2(t)$  as state variables and  $v_c(t)$  as output.

- 1) Find the state space equation for the RLC system

We can start by expressing our state variables using Kirchoff's Voltage law.

$$V_s(t) = V_r(t) + V_c(t) + V_l(t)$$

$$V_s(t) = iR + V_c(t) + L \frac{di}{dt}$$

$$\frac{dV_c}{dt} = \frac{i}{C}$$

Rewriting these in terms of our state variables we get the state equation.

$$\dot{x}_1 = \frac{x_2}{C}$$

$$\dot{x}_2 = \frac{1}{L}(V_s(t) - x_2R - x_1)$$

$$y = x_1$$

$$\mathbf{A} = \begin{bmatrix} 0 & \frac{1}{C} \\ -\frac{1}{L} & -\frac{R}{L} \end{bmatrix} \quad \mathbf{B} = \begin{bmatrix} 0 \\ \frac{1}{L} \end{bmatrix} \quad \mathbf{C} = [1 \quad 0] \quad \mathbf{D} = [0 \quad 0]$$

Plugging in our values

$$\mathbf{A} = \begin{bmatrix} 0 & 1 \\ -5 & -6 \end{bmatrix} \quad \mathbf{B} = \begin{bmatrix} 0 \\ 5 \end{bmatrix} \quad \mathbf{C} = [1 \quad 0] \quad \mathbf{D} = [0 \quad 0]$$

- 2) If  $v_c(0) = 0, i_l(0) = 5, v_s(t) = 0$ , find the  $\mathbf{x}(t)$  for the system

$$\mathbf{x}(t) = e^{\mathbf{A}t} \mathbf{x}(0) + \int_0^t e^{\mathbf{A}(t-\tau)} \mathbf{B} \mathbf{u}(\tau) d\tau$$


$$\mathbf{x}(0) = \begin{bmatrix} 0 \\ 5 \end{bmatrix}$$

$$e^{\mathbf{A}t} = \begin{bmatrix} .25e^{-1t} - 0.25e^{-5t} & 0.25e^{-1t} - 0.25e^{-5t} \\ 1.25e^{-5t} - 1.25e^{-1t} & 1.25e^{-5t} - 0.25e^{-1t} \end{bmatrix}$$

$$e^{\mathbf{A}t} \mathbf{x}(0) = \begin{bmatrix} 1.25e^{-1t} - 1.25e^{-5t} \\ 6.25e^{-5t} - 1.25e^{-1t} \end{bmatrix}$$

$$\mathbf{u} = 0 \implies e^{\mathbf{A}(t-\tau)} \mathbf{B} \mathbf{u} = 0$$
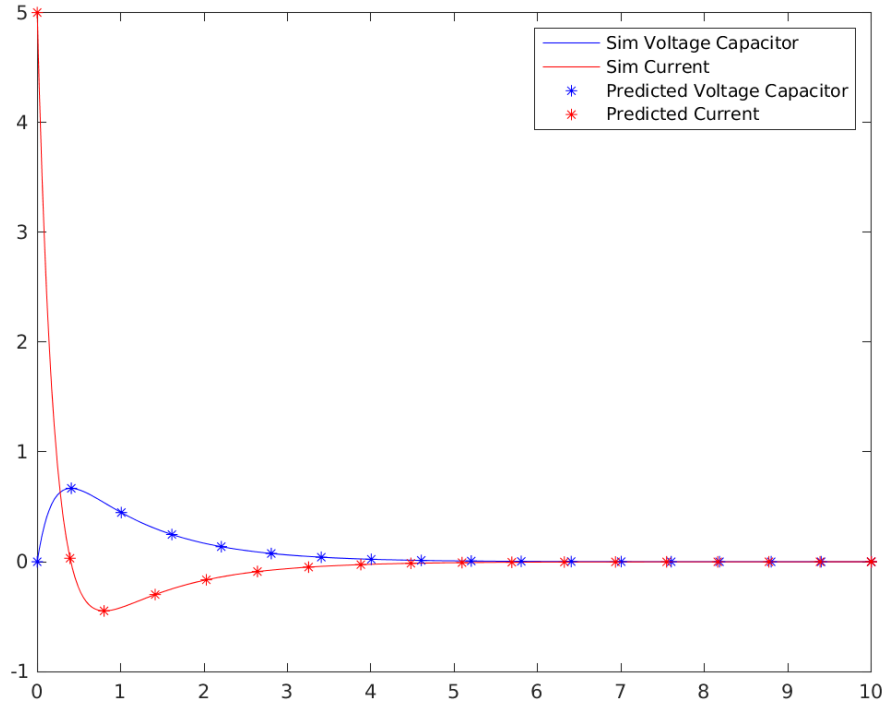
$$\Rightarrow \mathbf{x}(t) = \begin{bmatrix} 1.25e^{-1t} - 1.25e^{-5t} \\ 6.25e^{-5t} - 1.25e^{-1t} \end{bmatrix}$$



3) If  $v_c(0) = 0, i_l(0) = 0, v_s(t) = 5$ , find the  $y(t)$  for the system

We have mostly the same situation just a few parameters have changed.

$$x(0) = \begin{bmatrix} 0 \\ 0 \end{bmatrix} \quad v_s \neq 0$$


So we must evaluate the convolution.

$$\int_0^t e^{\mathbf{A}(t-\tau)} \mathbf{B} \mathbf{u}(\tau) d\tau = \begin{bmatrix} 5 + 1.25e^{-5t} - 6.25e^{-1t} \\ -1.7763 * 10^{-15} - 6.25e^{-5t} + 6.25e^{-1t} \end{bmatrix} = x(t)$$

And since the initial condition is zero the state variables are just the convolution.

$$y(t) = \mathbf{C}x(t)$$

$$y(t) = 5 + 1.25e^{-5t} - 6.25e^{-1t}$$

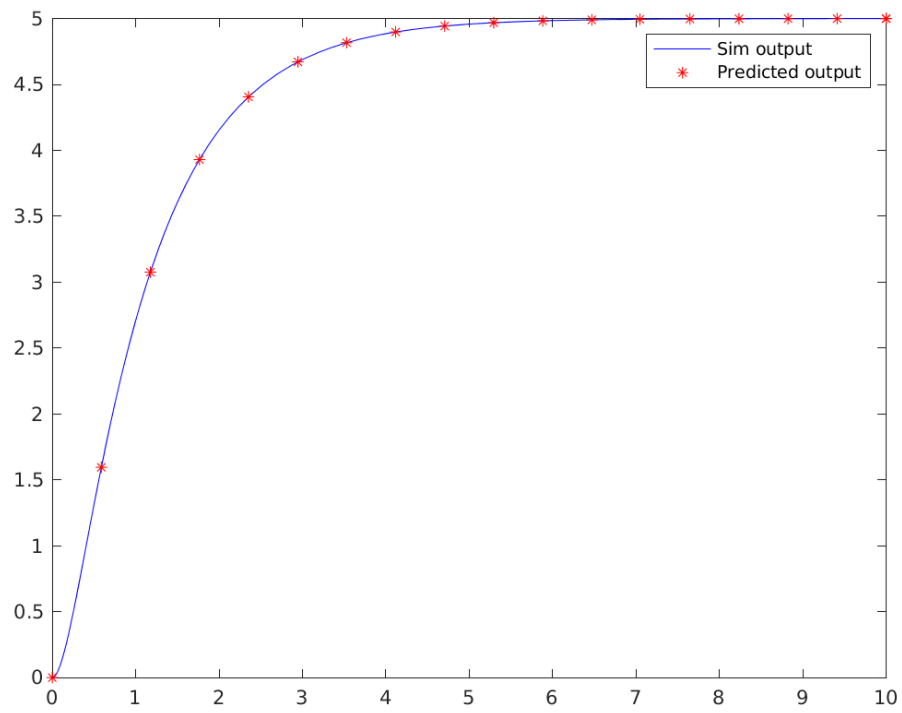

### Problem 3

Consider the system

$$\ddot{x} + 4\dot{x} + 4x = u$$

- 1) Find the state space model for the system

Let  $x_1 = x$  and  $x_2 = \dot{x}$

$$\dot{x} = \begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} x_2 \\ -4x_2 - 4x_1 + u \end{bmatrix}$$

$$\mathbf{A} = \begin{bmatrix} 0 & 1 \\ -4 & -4 \end{bmatrix} \quad \mathbf{B} = \begin{bmatrix} 0 \\ 1 \end{bmatrix} \quad \mathbf{C} = [1 \quad 0] \quad \mathbf{D} = [0 \quad 0]$$

- 2) Find the transfer function for the system. (Hint: you can use  $\mathbf{C}(s\mathbf{I} - \mathbf{A}^{-1})\mathbf{B} + D$ )

$$s\mathbf{I} - \mathbf{A} = \begin{bmatrix} s & -1 \\ 4 & s+4 \end{bmatrix} \implies (s\mathbf{I} - \mathbf{A})^{-1} = \frac{1}{s^2 + 4s + 4} \begin{bmatrix} s+4 & 1 \\ -4 & s \end{bmatrix}$$

$$\hat{\mathbf{x}}(s) = \frac{1}{s^2 + 4s + 4} [1 \quad 0] \begin{bmatrix} s+4 & 1 \\ -4 & s \end{bmatrix} \begin{bmatrix} 0 \\ 1 \end{bmatrix} = \frac{1}{s^2 + 4s + 4}$$

$$\hat{\mathbf{x}}(s) = \frac{1}{s^2 + 4s + 4}$$

- 3) Suppose  $u(t) = e^{-2t} \sin(t)$  for  $t \geq 0$ , and  $\ddot{x}(0) = \dot{x}(0) = 0$ . Find the solution  $x(t)$

We want to use  $\hat{\mathbf{y}}(s) = \hat{\mathbf{G}}(s)\hat{\mathbf{u}}(s)$  where  $\hat{\mathbf{G}}(s)$  is what we computed in part 2. First we must find the input's representation in the laplace space.

$$\hat{\mathbf{u}}(s) = \mathcal{L}\{e^{-2t} \sin(t)\} = \frac{1}{s^2 + 4s + 5} \quad t > 0$$

$$\hat{\mathbf{y}}(s) = \frac{1}{s^2 + 4s + 5} \frac{1}{s^2 + 4s + 4} = \frac{1}{(2+s)^2(5+4s+s^2)}$$

$$y(t) = \mathcal{L}^{-1}(\hat{\mathbf{y}}) = e^{-2t}(t - \sin(t))$$

